

1) Simplify -

$$Y = \overline{A}CD + \overline{B}(\overline{C+A(BD)}) + \overline{A}B\overline{C}\overline{D}$$

$$= \overline{A}CD + \overline{B} + (\overline{C+A(BD)}) + \overline{A}B\overline{C}\overline{D}$$

$$= \overline{A}CD + \overline{B} + C + A\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D}$$

$$= \overline{A}CD + \overline{B} + C + \overline{A}B + \overline{A}C + \overline{A}B\overline{C}\overline{D}$$

$$= \overline{A}CD + \overline{B}(A+1) + C + \overline{A}C + \overline{A}B\overline{C}\overline{D}$$

$$= \overline{A}CD + \overline{B} + C + \overline{A}C + \overline{A}B\overline{C}\overline{D}$$

$$\geq \overline{A} + \overline{C} + \overline{D} + \overline{B} + C + \overline{A}C + \overline{A}B\overline{C}\overline{D}$$

$$= \overline{A}[1 + \overline{B}C\overline{D}] + \overline{C} + C + \overline{A}C + \overline{D} + \overline{B}$$

$$= \overline{A} + \overline{C}(A+1) + C + \overline{D} + \overline{B}$$

$$= \overline{A} + \overline{C} + C + \overline{D} + \overline{B}$$

$$= 1 + \overline{A} + \overline{D} + \overline{B}$$

$$= 1$$

$\therefore Y = 1$

2) $Z = A\overline{B} + \overline{A}CD + \overline{A}\overline{B}C + \overline{A}\overline{B}C\overline{D}$

$$= A\overline{B}(C + \overline{C}) + \overline{A}CD(B + \overline{B}) + \overline{A}\overline{B}C(D + \overline{D}) + \overline{A}\overline{B}C\overline{D}$$

$$= (A\overline{B}C + A\overline{B}\overline{C}) + \overline{A}CD(B + \overline{B}) + \overline{A}\overline{B}C(D + \overline{D}) + \overline{A}\overline{B}C\overline{D}$$

$$= A\overline{B}C + A\overline{B}\overline{C} + \overline{A}CD + \overline{A}C\overline{D} + \overline{A}\overline{B}C + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}C\overline{D}$$


$$\sum_m \{11, 10, 9, 8, 7, 5, 5, 6, 10\}$$

$$= \sum_m \{11, 10, 9, 8, 7, 5, 6\}$$

$$\leq \sum_m \{5, 6, 7, 8, 9, 10, 11\}$$

$$4 \ 5 \quad 0101 \quad 0111 \quad 1111 \\ = 8 + 4 + 2 + 1$$

AB \ CD	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

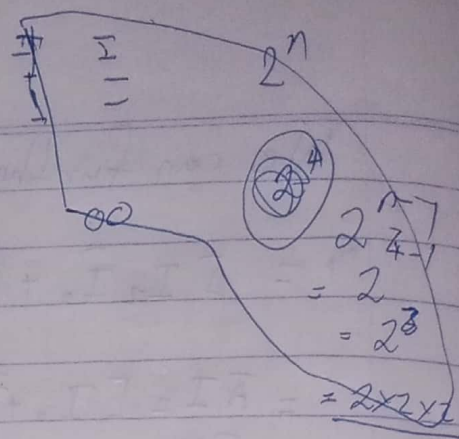

$$Y = A\bar{B} + \bar{A}BD + \bar{A}BC$$

$$Y = A\bar{B} + \bar{A}BD + \bar{A}BC$$

③ Multiplexer. → Multiplexer or Mux is a digital switch. This is also known as data selector. It is a combinational circuit with 2^n inputs where $n \geq 0$, n selector lines and one output. Selector lines are used to select or map one particular input to the output.

The 2×1 Multiplexer is an example.

$$A \Rightarrow n, n=1$$


$$2^n = 2^1 = 2$$

$$n = 2 = A$$

$$\text{Output} = Y$$

$$\text{Inputs: } I_1, I_0$$

Selector A	Inputs		Output Y
	I_1	I_0	
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

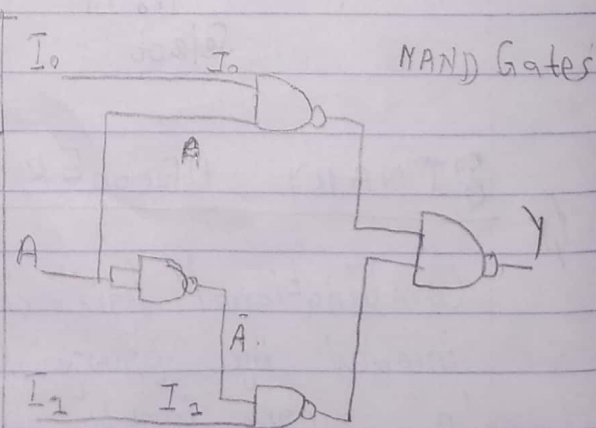

A acts as a selector between the two I_0 and I_1 inputs for output Y.

We can further prove this by boolean expression

$$\begin{aligned}
 Y &= \bar{A} I_2 \bar{I}_0 + \bar{A} I_1 I_0 + A \bar{I}_0 \bar{I}_1 + A I_0 I_1 \\
 &= \bar{A} I_1 [I_0 + \bar{I}_0] + A I_0 [\bar{I}_1 + I_1] \\
 &= \bar{A} I_1 + A I_0
 \end{aligned}$$


The procedure can be used for any 2^n inputs by 1 output multiplexer

Thus for $n=2$,

$$\text{Inputs} = 2^2 = 4$$

$$\text{Selector lines} = 2$$

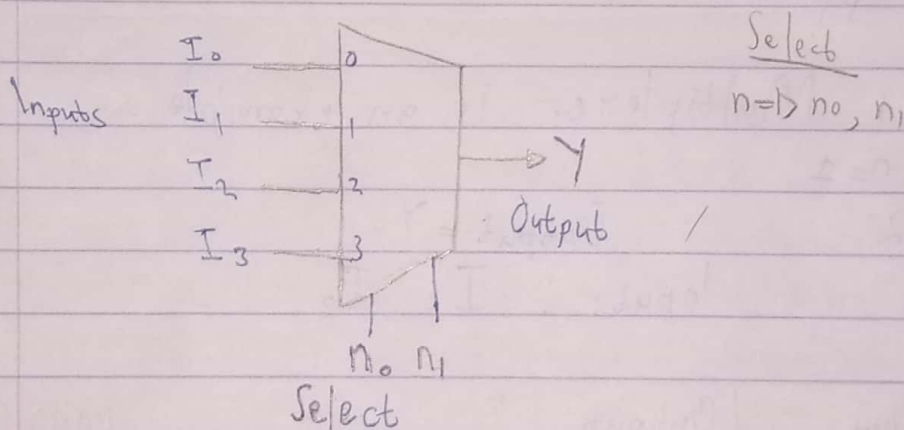The multiplexer can be represented by a symbol.



BINARY DECODER


Combinational logic circuit that decodes messages encoded by binary encoder. Binary decoder transforms 'n' binary inputs into 2^n outputs. n inputs activate one and only one of 2^n outputs.

Example 2 x 4 Binary Decoder using AND gates

$n = 2$

A	B	Q_0	Q_1	Q_2	Q_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

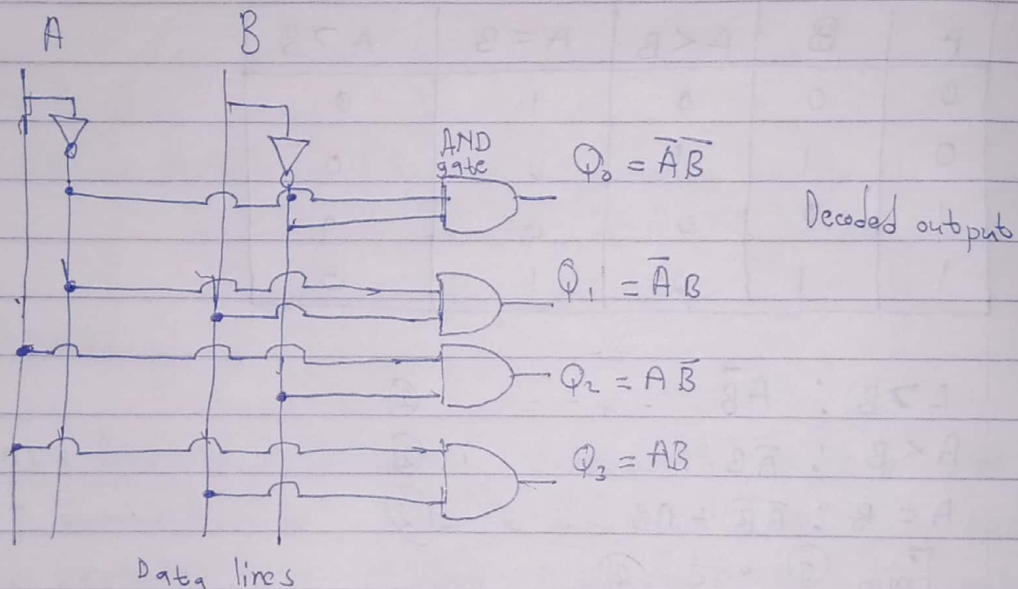Each output represents one of the minterms of the input variables A, B.




A NAND gate combinations circuit acts as only one output equal to logic '0' with all others '1' at any given time.

MAGNITUDE COMPARATOR → combinational circuit that compares two digital or binary numbers to find out if one is equal, greater or lesser than the other.

For instance input A and B have three output terminals $A > B$, $A = B$ and $A < B$ functions.

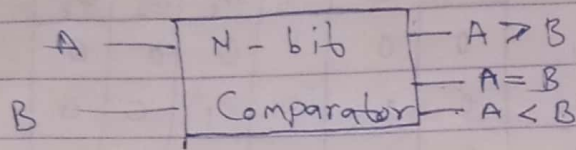This block diagram demonstrates the definition above.



1-Bit Magnitude Comparator

A comparator for comparing two bits is called a single-bit comparator.

1 bit comparator truth table

A	B	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

$$A > B : \bar{A}B \quad \text{--- (1)}$$

$$A < B : A\bar{B} \quad \text{--- (2)}$$

$$A = B : \bar{A}\bar{B} + AB \quad \text{--- (3)}$$

From (1) and (2)

$$(A < B) + (A > B) = \bar{A}B + A\bar{B}$$

$$((A < B) + (A > B))' = (\bar{A}B + A\bar{B})'$$

$$= (\bar{A}\bar{B})(\bar{A}B)$$

$$= (\bar{A} + B)(A + \bar{B})$$


$$= \bar{A}A + \bar{A}\bar{B} + AB + B\bar{B}$$

$$= \bar{A}\bar{B} + AB$$

Thus

$$((A < B) + (A > B))' = (A = B)$$

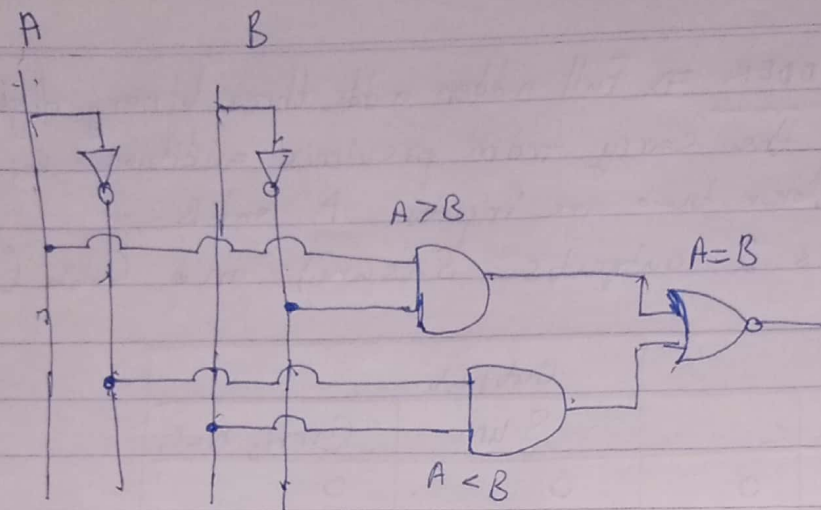Single-bit Comparator Combinational Circuit



For an n -bit comparator the number of combinations are

$$A = B : 2^n$$

$$A > B \text{ or } A < B : \frac{(2^{2n} - 2^n)}{2}$$

ADDERS


HALF ADDER - Electronic circuit that performs addition of numbers. It is able to add two single binary digits and provide the output plus a carry value. Two inputs A and B , and two outputs S and C .
 S (sum), C (carry)

Half adder Truth table.

Inputs		Outputs	
A	B	C	S
0	0	0	0
1	0	0	1
0	1	0	1
1	1	1	0

$$S = A\bar{B} + \bar{A}B = A \oplus B$$

$$C = AB$$

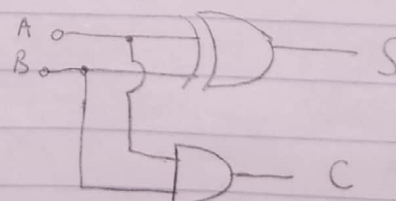


Full ADDER \Rightarrow Full adder adds three binary digits
 One is the carry from previous addition C_{in} .
 The other two are inputs A and B.
 It has 2 outputs S (sum) and C_{out} (carry output).

Input			Output	
A	B	C	Sum	Carry Out
0	0	0	0	0
1	1	1	1	1
0	1	1	0	1
1	0	1	0	1
0	0	1	1	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1

$$Carry\ out = AB + BC_{in} + AC_{in}$$



$$Sum = (A \oplus B) \oplus C_{in}$$

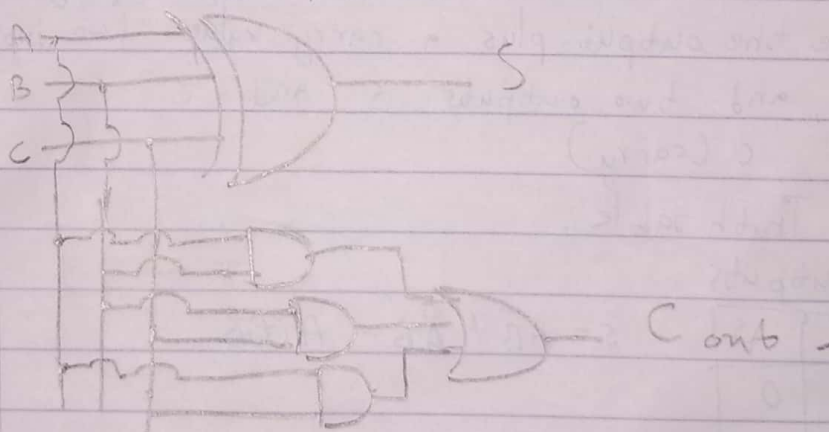

4) Sequential logic circuit of two JK FF's. Initially Cleared obtain the output Q_1 and Q_0 for 5 clock.

Truth table for JK flipflop

J	K	Q_{n+1}	Clock
0	0	Q [No change]	↑
0	1	0 [Reset]	↑
1	0	1 [Set]	↑
1	1	\bar{Q} [Toggle]	↑

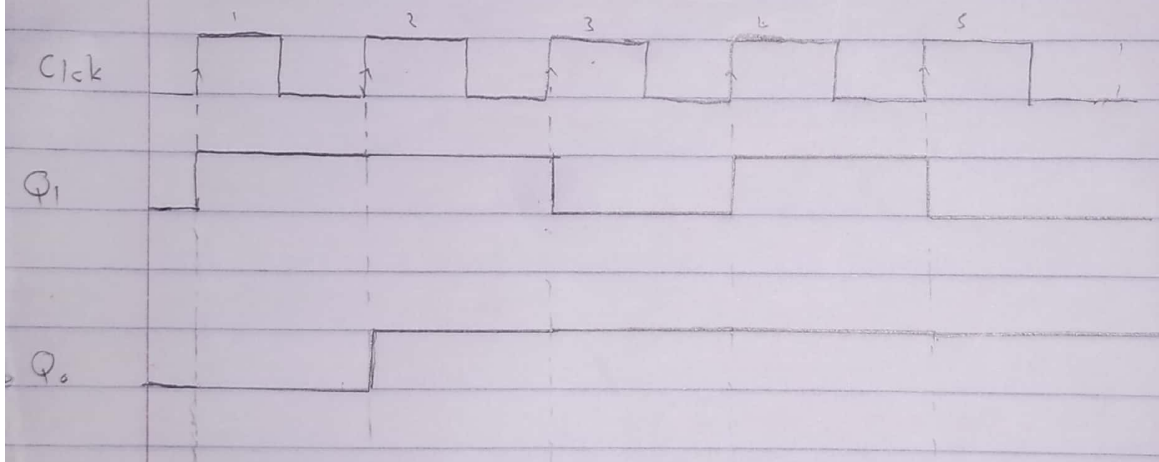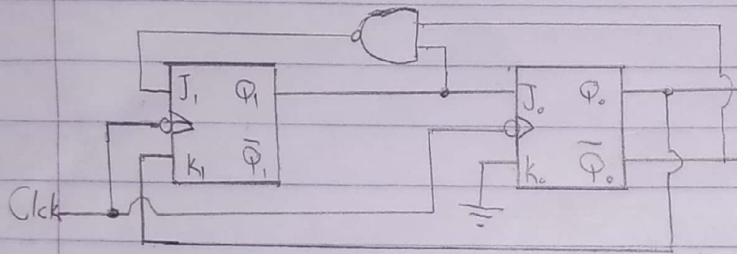

Clock	Q_1	Q_0
0	0	0
1	1	0
2	1	1
3	0	1
4	1	1
5	0	1